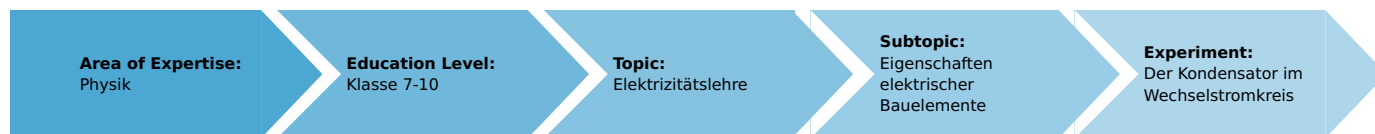


Capacitors in alternating current circuits (Item No.: P1373600)

Curricular Relevance



Difficulty



Intermediate

Preparation Time



10 Minutes

Execution Time



10 Minutes

Recommended Group Size



2 Students

Additional Requirements:

Experiment Variations:

Keywords:

Task and equipment

Information for teachers

Additional information

The students should recognize that a capacitor represents a finitely large resistance in an alternating current circuit. The two experiments suggested are intended to result in qualitative and semi-quantitative statements on capacitive resistance.

Notes on setup and procedure

In the second experiment, through the operation of the changeover switch, an alternating current flows despite the direct voltage in the branch of the circuit containing the capacitor and the lamp. It is preferable to bring the students to understand this from theoretical considerations before they carry out the experiment.

Remarks

The resistance that a capacitor causes in an alternating current circuit is termed the capacitive resistance X_C . The following is valid:

$$X_C = 1/(\omega \cdot C) = 1/(2\pi \cdot f \cdot C).$$

If there is only one capacitive resistance in an alternating current circuit alongside the ohmic resistance, then, for the alternating current resistance with sinusoidal alternating current:

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{R^2 + (1/(\omega C))^2}$$


Capacitors in alternating current circuits (Item No.: P1373600)

Task and equipment

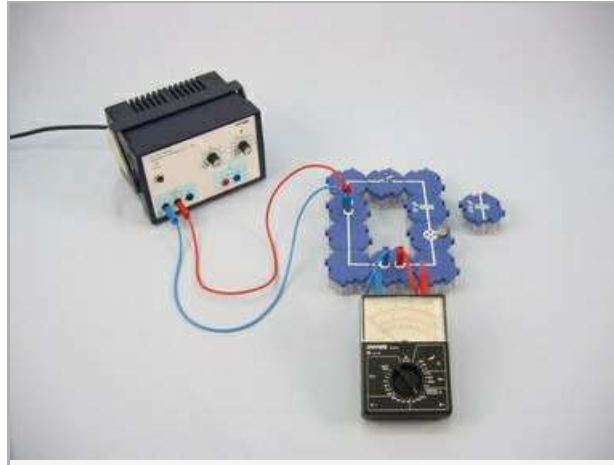Task

How does a capacitor act in an alternating current circuit?

Prove that a capacitor does not interrupt an alternating current circuit, and examine on what the current is dependent in an alternating current circuit containing a capacitor.



Equipment



Position No.	Material	Order No.	Quantity
1	Straight connector module, SB	05601-01	4
2	Angled connector module, SB	05601-02	4
3	T-shaped connector module, SB	05601-03	1
4	Interrupted connector module, SB	05601-04	2
5	Junction module, SB	05601-10	2
6	On-off switch module, SB	05602-01	1
7	Change-over switch module, SB	05602-02	1
8	Socket module for incandescent lamp E10, SB	05604-00	2
9	Capacitor module 47 μ F non-polar electrolytic, SB	05645-47	1
10	Capacitor module 470 μ F non-polar electrolytic, SB	05646-47	1
11	Connecting cord, 32 A, 250 mm, red	07360-01	1
12	Connecting cord, 32 A, 250 mm, blue	07360-04	1
13	Connecting cord, 32 A, 500 mm, red	07361-01	1
14	Connecting cord, 32 A, 500 mm, blue	07361-04	1
15	Filament lamps 4V/0.04A, E10, 10	06154-03	1 piece
15	Filament lamp 6 V/3 W, E10, 10 pcs.	35673-03	1 piece
16	Multi-range meter, analogue	07028-01	1
17	PHYWE power supply DC: 0...12 V, 2 A / AC: 6 V, 12 V, 5 A	13506-93	1

Set-up and procedure

Set-up

First experiment

Set up the circuit as shown in Fig. 1 and Fig. 2, with the on/off switch open; make connection to the 6 V~ alternating voltage source and set it to measurement range 300 mA~.

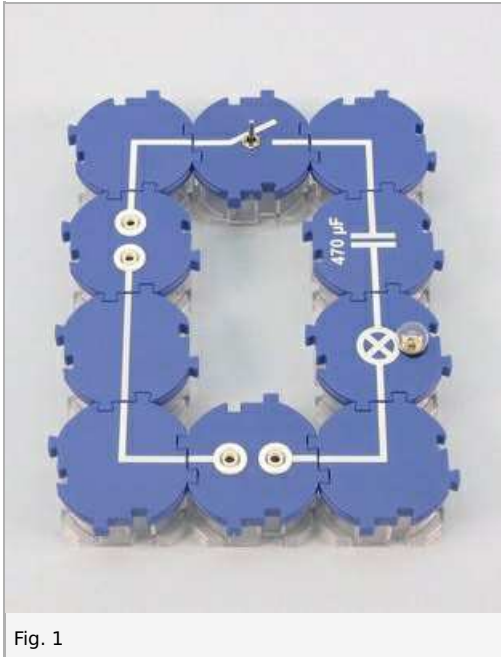


Fig. 1

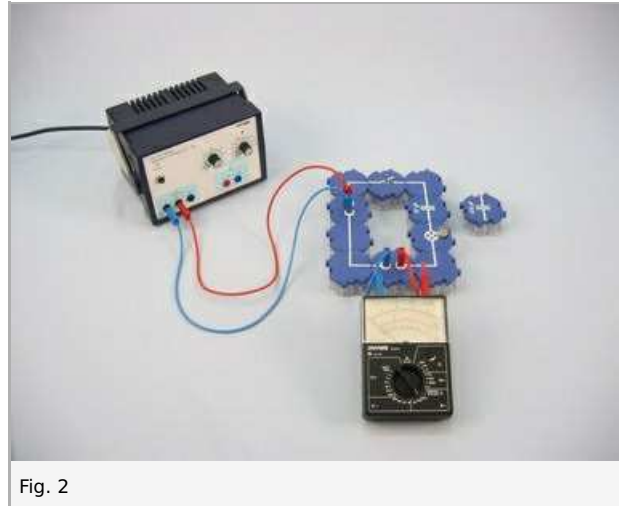


Fig. 2

Second experiment

Set up the circuit as shown in Fig. 3 and Fig. 4, with the on/off switch first open; turn the changeover switch to position 1 and set the power supply to 10 V direct voltage; prior to inserting the capacitor in the circuit, discharge it by short-circuiting it.

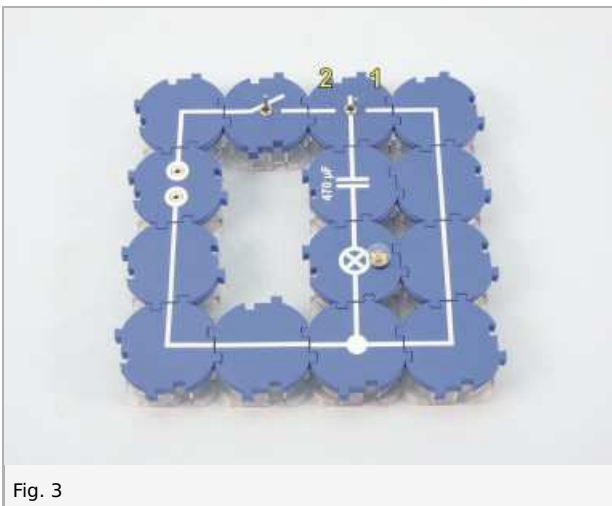


Fig. 3

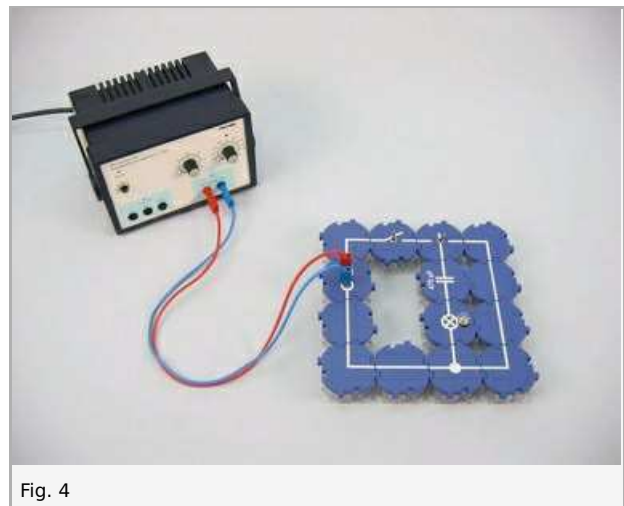


Fig. 4

Procedure

First experiment

- Close the alternating current circuit, measure the current and observe the brightness of the lamp; enter your observation and the measured value in Table 1 in the report.
- Change the measurement range to 3 A~.
- Replace the 47 μF capacitor with the 470 μF capacitor, measure the current and note the value (Table 1).
- Replace the capacitor with a connector module, measure the current and note the value (Table 1).
- Switch off the power supply.

Second experiment

- Switch on the power supply, close the circuit and observe the lamp; note what you observe under Result - Observations 1.
- Replace the 470 μF capacitor with the 47 μF capacitor (Fig. 5); operate the changeover switch, first slowly, then in ever quicker succession (with increasing switching frequency), and observe the lamp; note what you observe under Result - Observations 2.
- Switch off the power supply.

Report: Capacitors in alternating current circuits

Result - Table 1

Note your observations.

	Lamp lights up		Current I in mA
47 μF capacitor	not at all	1	1 ± 0
470 μF capacitor	brightly	1	1 ± 0
no capacitor	even more brightly	1	1 ± 0

Result - Observations 1

Note your observations.

.....

.....

.....

.....

Result - Observations 2

Note your observations.

.....

.....

.....

.....

Evaluation - Question 1

Capacitors in direct current circuits represent an infinitely large resistance, as they interrupt the circuit. What follows from the results of the first experiment entered in Table 1?

.....

.....

.....

.....

Evaluation - Question 2

What can you state, from the observations noted under Observations 2, on the relationship between the resistance of a capacitor in an alternating current circuit and the frequency?

.....

.....

.....

.....

Evaluation - Question 3

Summarise and explain the combined results of the two experiments.

.....

.....

.....

.....