

# The current-voltage characteristic of an NPN transistor

(Item No.: P1374400)

## Curricular Relevance



### Difficulty



Intermediate

### Preparation Time



10 Minutes

### Execution Time



10 Minutes

### Recommended Group Size



2 Students

### Additional Requirements:

### Experiment Variations:

### Keywords:

## Task and equipment

## Information for teachers

## Additional information

The knowledge of the characteristics of a transistor is a prerequisite for a deeper understanding of the processes related to a transistor amplifying or switching stage. Of the four characteristics (the output, control, input and reverse voltage transfer ratio characteristics), the output and control characteristics are particularly important. This experiment is therefore limited to the recording of the characteristic curves for control and output. The other characteristic curves can be determined by slightly altering the experimental setup.

We recommend some class time to be spent after the experiment going over the characteristic curves that the students recorded. The operating lines graphed in the output characteristic field can be used to deepen their understanding of the control process. For example, you can explain voltage gain as a function of load resistance, the oppositional nature of output and input voltage, the output power achievable, and the influence of the position of the operating point on signal clippings.

## Notes on setup and procedure

When care is taken that the polarity of the connections to the measuring instruments and the diode is correct, no great difficulty should be experienced in setting up the circuit.

As changes in the collector voltages influence the strength of the base current, the collector voltage is held constant and the collector current measured in dependence on the base current. Take care that the maximum power dissipation of the transistors  $P_D = 600 \text{ mW}$  is not exceeded. This is ensured when the collector current is kept below 50 mA.

# The current-voltage characteristic of an NPN transistor


(Item No.: P1374400)

## Task and equipment

### Task
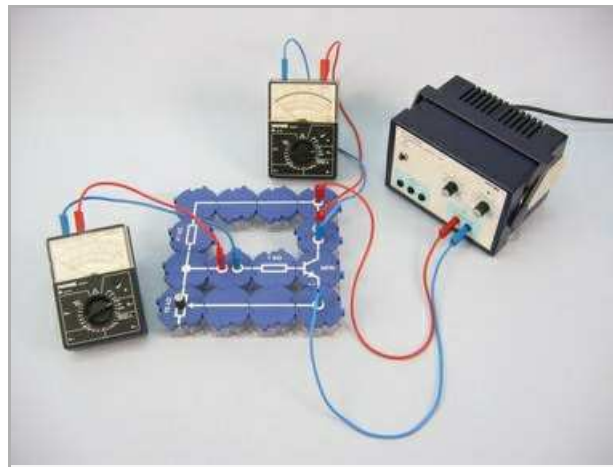
#### How does the collector current of a transistor depend on the base current and collector voltage?

Examine the dependence of the collector current of an npn transistor on the base current at various collector voltages.



Equipment



Position No.	Material	Order No.	Quantity
1	Straight connector module, SB	05601-01	4
2	Angled connector module, SB	05601-02	1
3	T-shaped connector module, SB	05601-03	1
4	Interrupted connector module, SB	05601-04	2
5	Angled connector module with socket, SB	05601-12	2
6	Resistor module 47 kOhm, SB	05615-47	1
7	Resistor module 10 kOhm, SB	05615-10	1
8	Resistor module 1 kOhm, SB	05614-10	1
9	Potentiometer module 10 kOhm, SB	05625-10	1
10	NPN transistor module BC337, SB	05656-00	1
11	Connecting cord, 32 A, 250 mm, red	07360-01	1
12	Connecting cord, 32 A, 250 mm, blue	07360-04	1
13	Connecting cord, 32 A, 500 mm, red	07361-01	2
14	Connecting cord, 32 A, 500 mm, blue	07361-04	2
15	PHYWE power supply DC: 0...12 V, 2 A / AC: 6 V, 12 V, 5 A	13506-93	1
16	Multi-range meter, analogue	07028-01	2

## Set-up and procedure

### Set-up

Set up the circuit as shown in Fig. 1 and Fig. 2, ensure that the measurement ranges and polarity of the measuring instruments are correctly chosen (measurement range 50  $\mu\text{A}$  for the base current, 30 mA for the collector current).

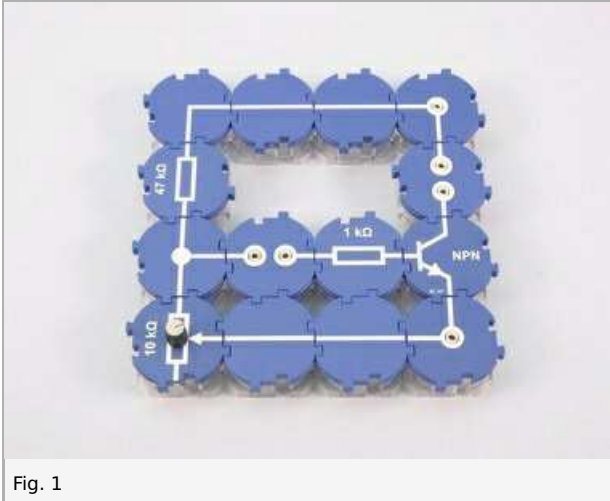


Fig. 1

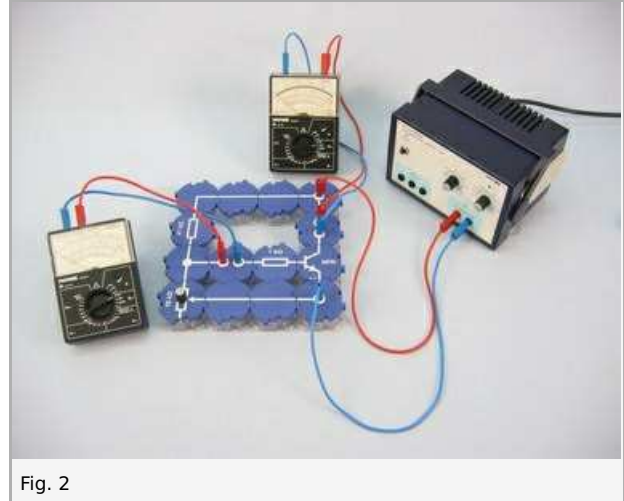


Fig. 2

### Procedure

- Turn the potentiometer to the right stop.
- Switch on the power supply; set the voltage on the power supply to  $U_{CE} = 12\text{ V}$ .
- Use the potentiometer to increase the base current in steps of  $I_B = 10\ \mu\text{A}$  (wait until the base current is constant, correct if necessary) and enter the values for the collector current  $I_C$  in the appropriate boxes in Table 1 in the report.
- Reduce the collector voltage in steps of 1 V; carry out the measurements and enter the results in Table 1.
- With voltages of  $U_{CE} = 6\text{ V}$  to  $U_{CE} = 2\text{ V}$ , replace the 47 k $\Omega$  resistor with a 10 k $\Omega$  resistor (Fig. 3).
- Finally set  $U_{CE} = 0\text{ V}$  and carry out the measurements.
- Switch off the power supply.

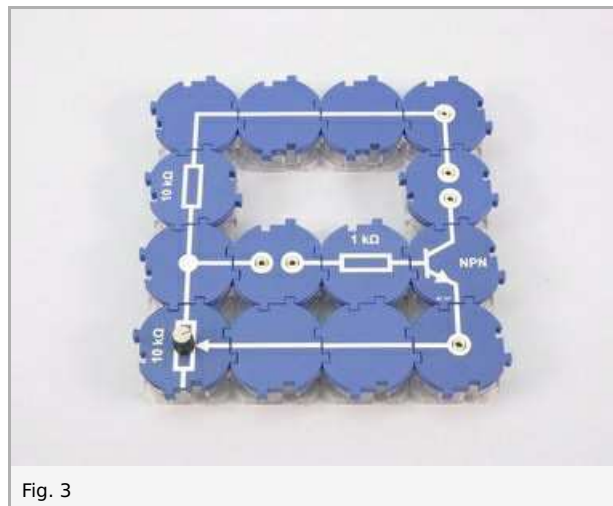


Fig. 3


# Report: The current-voltage characteristic of an NPN transistor

## Result - Table 1

Record the collector current  $I_C$  in dependence on the voltage  $U_{CE}$  at different base currents  $I_B$ .

$U_{CE}$ in V	$I_B$ in $\mu A$ :				
	10	20	30	40	50
12	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$
11	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$
10	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$
9	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$
8	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$
7	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$
6	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$
5	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$
4	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$
3	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$
2	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$
0	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$	1 $\pm 0$

Number1

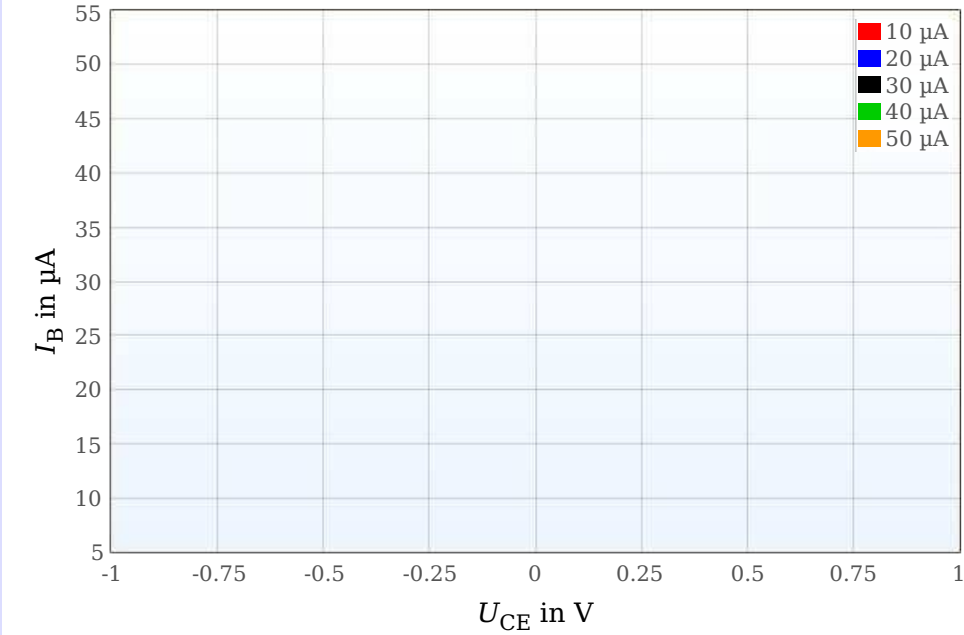

Evaluation - Question 1

The product of the collector voltage and collector current is the power dissipation  $P_D = U_C \cdot I_C$ . This is converted to heat by the transistor. Its maximal permissible value for the transistor used is 600 mW. Calculate the power dissipation of the transistor at a collector voltage of 5 V and a base current of 30  $\mu\text{A}$ , and check if the result lies below the maximal permissible value for  $P_D$ .

.....

.....

.....

.....

**Evaluation - Question 2**

The ratio  $\Delta U_{CE} / \Delta I_C$  is the output resistance of the transistor for a certain operating point.

Use the characteristic curve for a base current of  $30 \mu\text{A}$  to determine the change in the collector current  $\Delta I_C$  when the collector voltage  $\Delta U_{CE}$  is increased from 5 V to 10 V, and calculate the value of the output resistance of the transistor.

$\Delta I_C = \dots\dots\dots$  mA

$R = \Delta U_{CE} / \Delta I_C = \dots\dots\dots$  k $\Omega$